
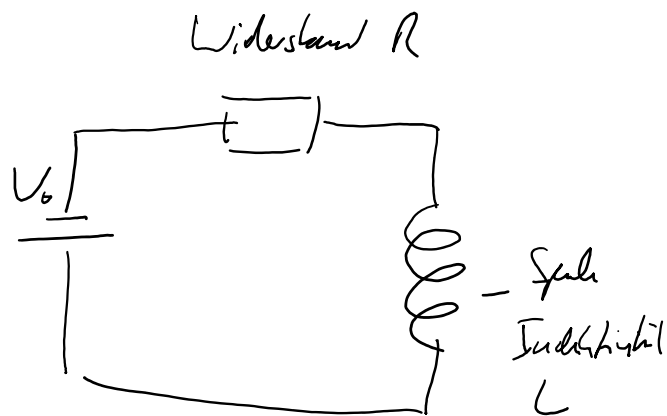


Wechselstromkreise

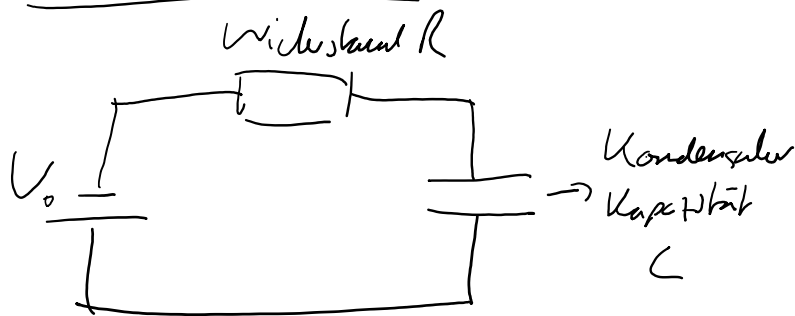

$$V_0 = RI + \frac{Q}{C}$$

$$= R \frac{dQ}{dt} + \frac{Q}{C}$$


$$\hookrightarrow \frac{dQ}{dt} = -\frac{1}{RC} Q$$

$$Q = Q_0 e^{-t/\tau} \quad \tau = RC$$

$$V_0 - L \frac{dI}{dt} = RI$$

$$\frac{dI}{dt} = -\frac{R}{L} I$$
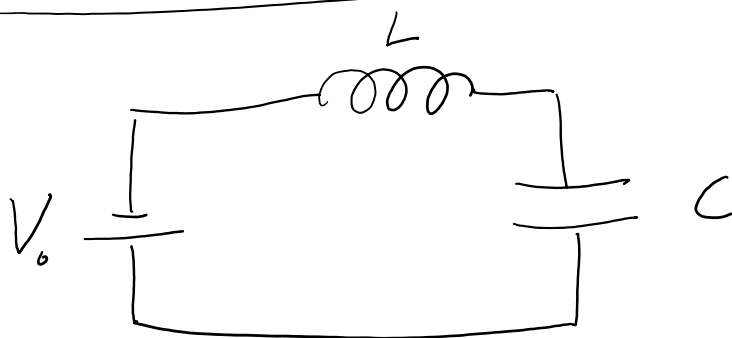
$$\hookrightarrow I = I_0 e^{-t/\tau} \quad \tau = \frac{L}{R}$$




$$V_0 - L \frac{dI}{dt} = \frac{Q}{C} \quad \left| \frac{d}{dt} \right.$$

$$\frac{dV_0}{dt} - L \frac{d^2 I}{dt^2} = \frac{I}{C}$$

$$\text{für } \frac{dV_0}{dt} = 0 \Rightarrow \frac{d^2 I}{dt^2} = -\frac{1}{LC} I = -\omega_s^2 I$$

$$\Rightarrow I = I_0 \cos(\omega_s t + \varphi)$$

$$\omega_s = \frac{1}{\sqrt{LC}}$$

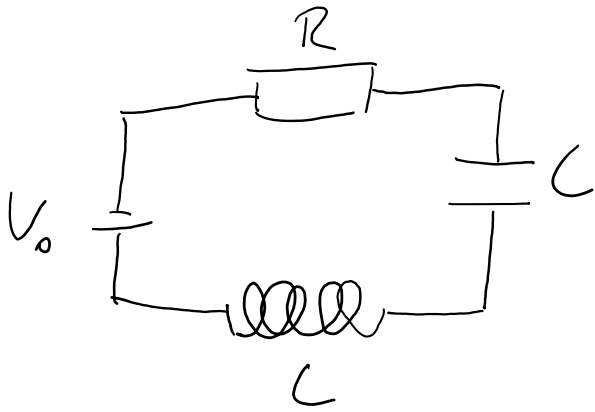

$$V_0 - L \frac{dI}{dt} = RI + \frac{Q}{C}$$

$$\frac{dV_0}{dt} = L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{I}{C}$$

$$\text{für } \frac{dV_0}{dt} = 0 \quad 0 = \frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I$$

$$0 = \frac{d^2 I}{dt^2} + 2\gamma \frac{dI}{dt} + \omega_0^2 I$$


$$2\gamma = \frac{R}{L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$I = I_0 e^{-at} \quad \Rightarrow \quad \frac{d^2 I}{dt^2} = a^2 I \quad \frac{dI}{dt} = -a I$$

$$a^2 I + 2\gamma(-a)I + \omega_0^2 I = 0$$

$$a^2 - 2\gamma a + \omega_0^2 = 0 \quad \Rightarrow \quad a = \frac{2\gamma \pm \sqrt{4\gamma^2 - 4\omega_0^2}}{2} = \gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

Resonanzkreis

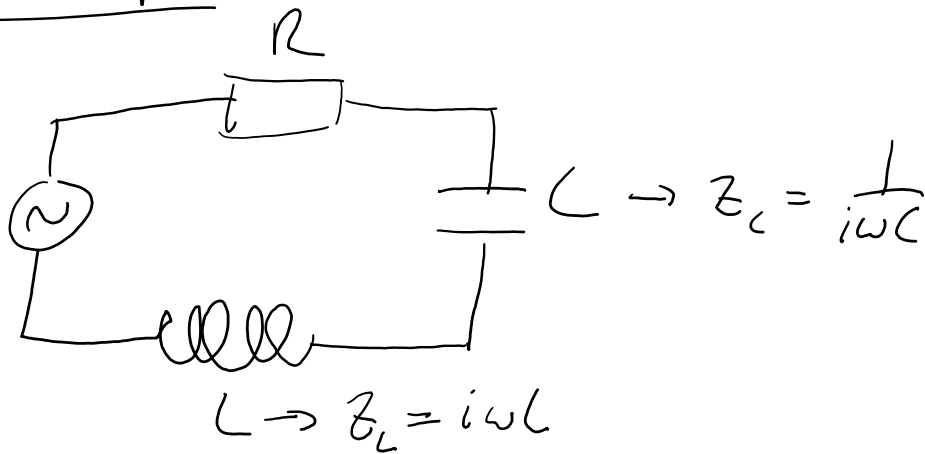

$$V_0 e^{i\omega t} = (R + z_C + z_L) \bar{I}_0 e^{i\omega t}$$

$$= \left(R + \underbrace{\frac{1}{i\omega C}}_{\int dt} + \underbrace{i\omega L}_{\frac{d}{dt}} \right) \bar{I}_0 e^{i\omega t}$$

$$\Rightarrow \bar{I}_0(t) = \frac{V_0 e^{i\omega t}}{R + \frac{1}{i\omega C} + i\omega L} = \frac{V_0 e^{i\omega t}}{i\omega L \left(\frac{R}{i\omega L} - \frac{1}{\omega^2 LC} + 1 \right)}$$

$$\frac{1}{LC} = \omega_0^2$$

$$= \frac{V_0 e^{i\omega t}}{i\omega L \left(\frac{R}{i\omega L} - \frac{\omega_0^2}{\omega^2} + 1 \right)}$$

$\omega = \omega_0 \rightarrow \text{Resonanz}$